

Homework 1

Monday, July 18, 2016 11:10 AM

Sean Webster

01446205


1. Sketch a gate-level design of 3:8 decoder (use labels throughout for clarity, include inverters for complementary signals)


a. Using AND gates


b. Using NAND gates only

c. Using NOR gates only

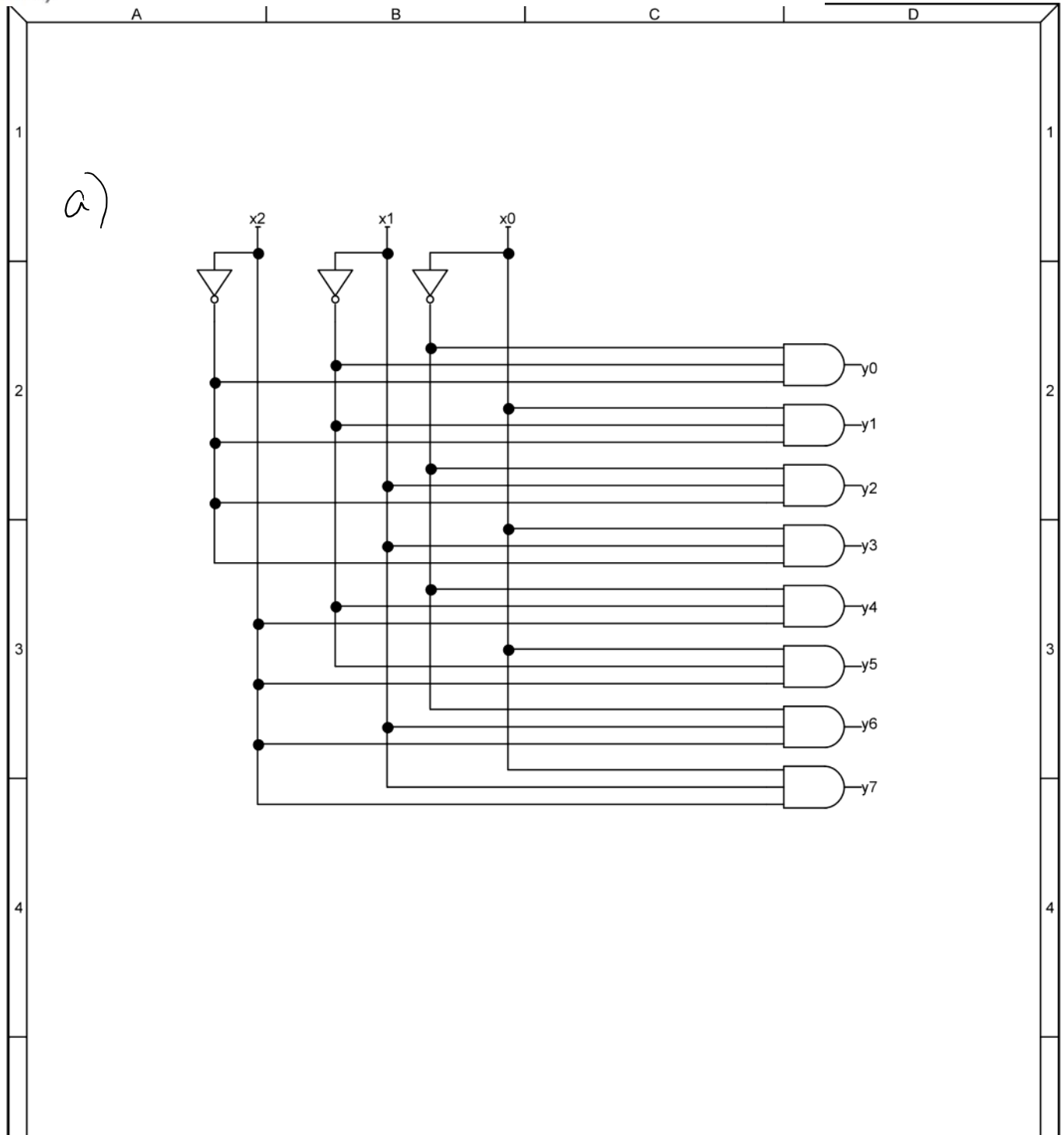
d. Comment on advantages or disadvantages of one design over others (min. two reasons)



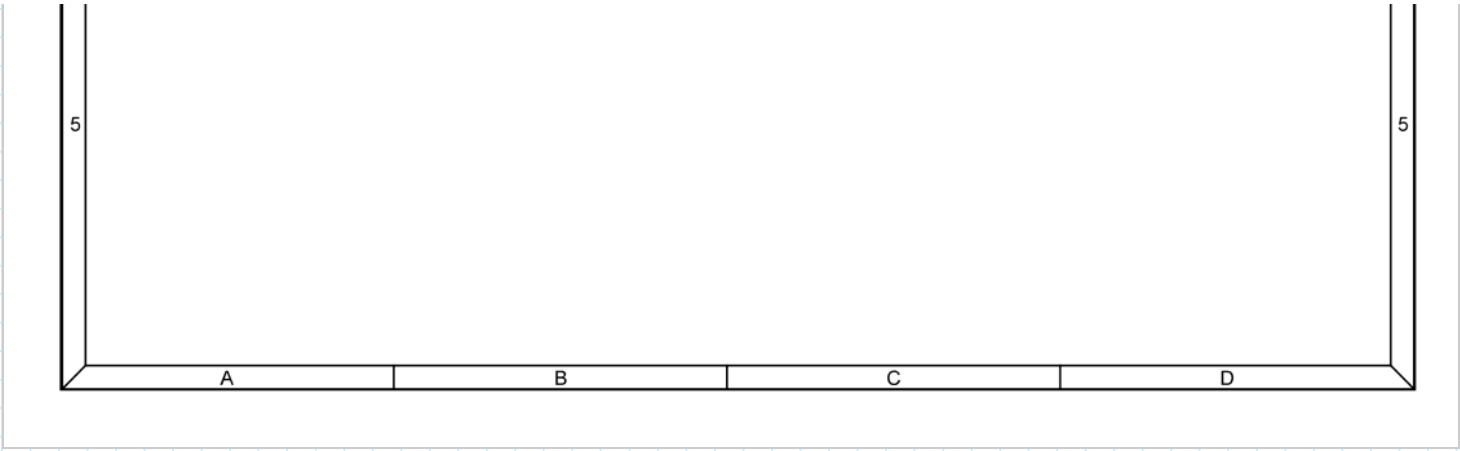

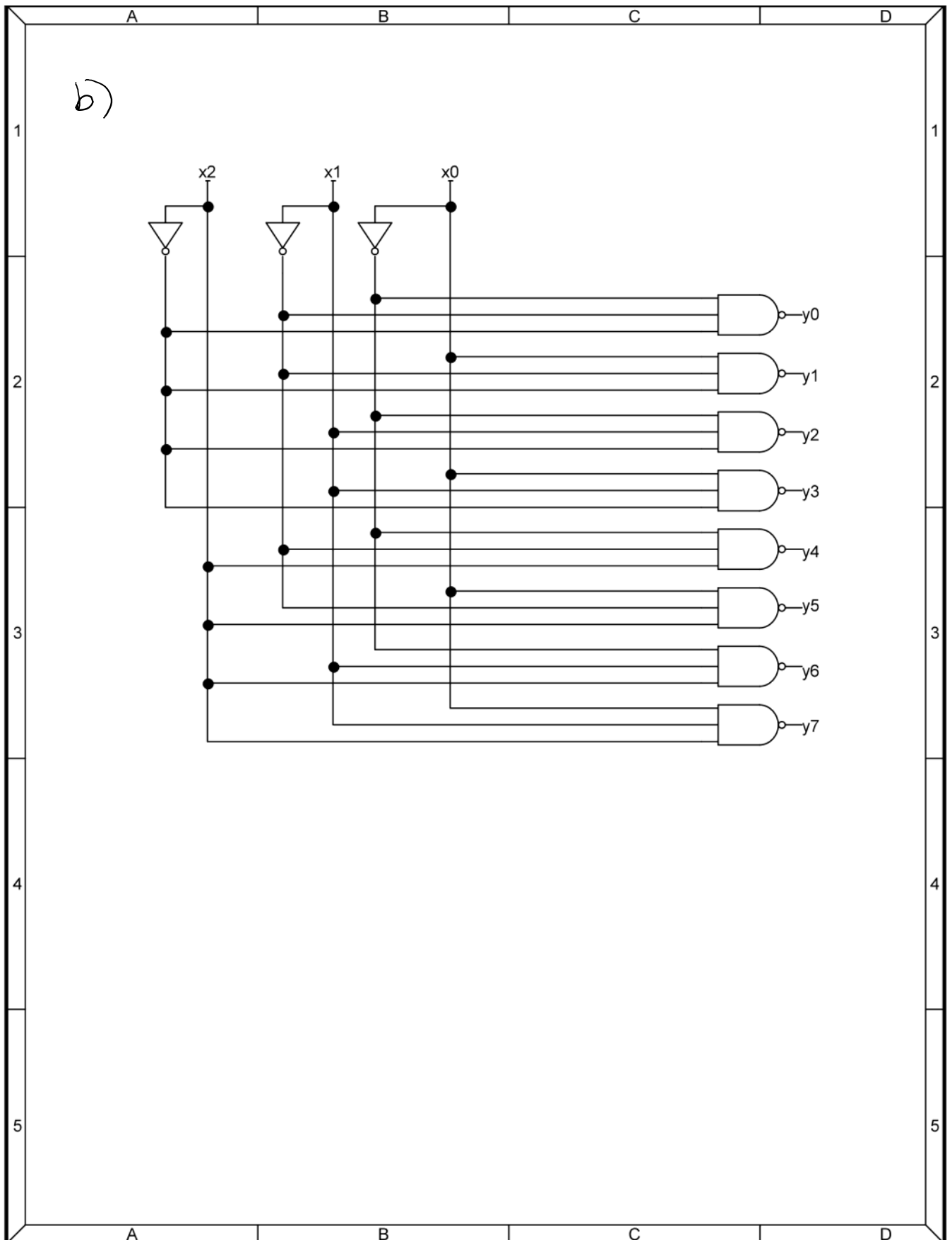


c)

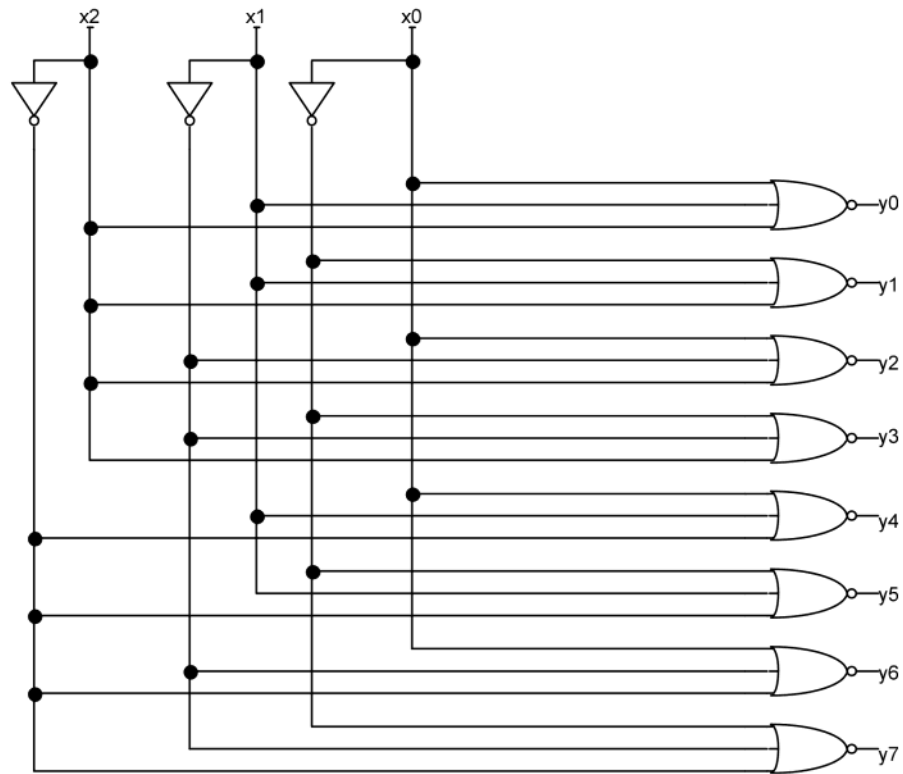

d)

A is the worst of these due to the fact that AND gates are more complex than NAND/NOR. This makes it slower, larger, and possibly out of synch with itself

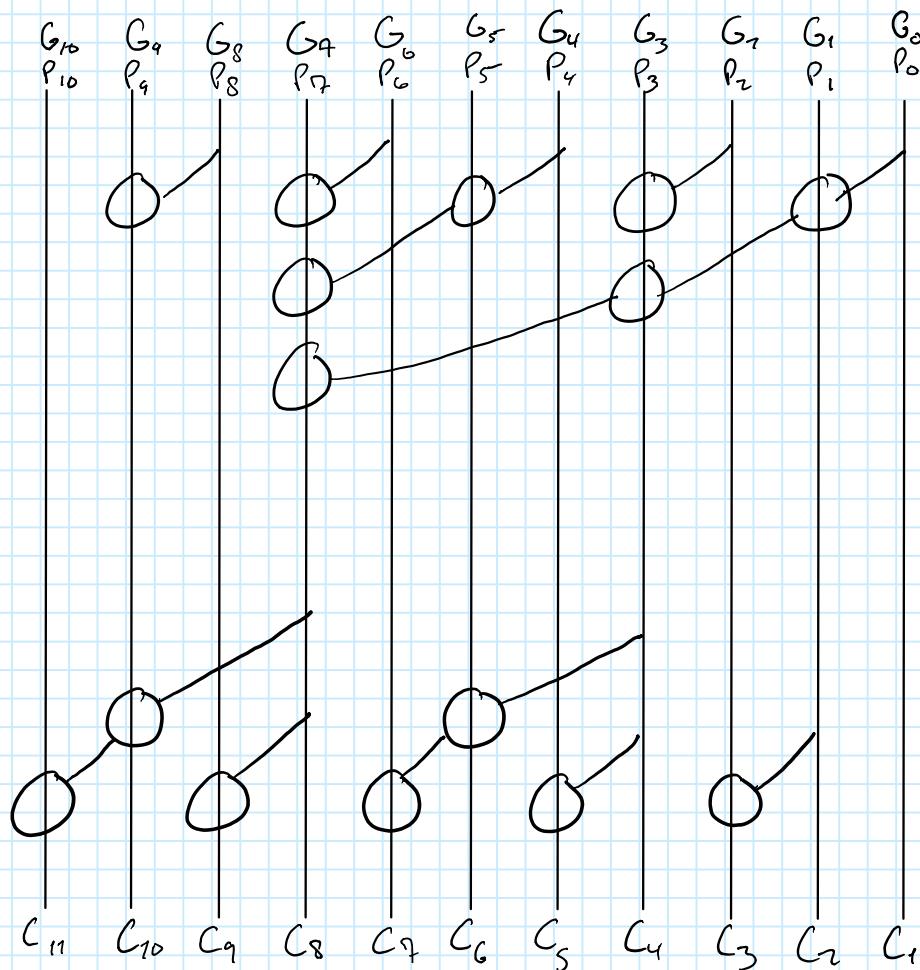2. Sketch a design of 11-bit Brent-Kung Adder. Make sure that the connections are clear and visible. (Use the example of 8-bit design from the class to help you figure out the 11-bit solution)



3. Perform a multiplication of the following floating point numbers in normalized IEEE single precision format:

- a. $6.25 \cdot -23.125$
b. $-17.875 \cdot -42.5$

a) 6.25×-23.125

$$6.25 \rightarrow 110.01 = 1.1601 \times 2^2$$

$$-23.125 \rightarrow 1011.001 = 1.011001 \times 2^4$$

$$0.25 \times 2 = 0.5$$
$$0.5 \times 2 = 1$$

$$\begin{aligned} 0.125 \times 2 &= 0.25 \\ 0.25 \times 2 &= 0.5 \\ 0.5 \times 2 &= 1 \end{aligned}$$

$$0.5 \times 2 = 1$$

0	1000 0001	1001 0000, ...
---	-----------	----------------

x

1	1000 0011	0111 0010 00...
---	-----------	-----------------

[illegible]

$$1.001000010001 \times 2^6$$

1 1000 0110 0010 0001 0001 0000...

$$.875 = \frac{\quad}{111}$$

$$0.75 \times 2 = 1.5$$

$$0.5 \times 2 = 1$$

$$17.875 \rightarrow 10001.111 \rightarrow 1.0001111 \times 2^4$$

$$42.5 \rightarrow 101010.1$$

$$1.010101 \times 2^5$$

$$\rightarrow 9 + 127 = 136 = 10001000$$

$$\begin{array}{r} 1,010101 \\ \times 1,000111 \\ \hline 1000111 \\ 1000111 \\ 1000111 \\ 1000111 \\ 1000111 \\ 1000111 \\ 1000111 \\ 1000111 \end{array}$$

1 0 1 1 1 0 1 1 1 0 1 1 →

0 1000 1000 0111 0111 011 00...