 



1. Identify the circuit below and determine what values it cycles through after asynchronous reset.

| cycle | Q0 | Q1 | Q2 | Q3 | TC |
|-------|----|----|----|----|----|
| 0     | 0  | 0  | 0  | 0  | 0  |
| 1     | 1  | 0  | 0  | 0  | 0  |
| 2     | 0  | 1  | 0  | 0  | 0  |
| 3     | 1  | 1  | 0  | 0  | 0  |
| 4     | 0  | 0  | 1  | 0  | 0  |
| 5     | 1  | 0  | 1  | 0  | 0  |
| 6     | 0  | 1  | 1  | 0  | 0  |
| 7     | 1  | 1  | 1  | 0  | 0  |
| 8     | 0  | 0  | 0  | 1  | 0  |
| 9     | 1  | 0  | 0  | 1  | 0  |
| 10    | 0  | 1  | 0  | 1  | 0  |
| 11    | 1  | 1  | 0  | 1  | 0  |
| 12    | 0  | 0  | 1  | 1  | 0  |
| 13    | 1  | 0  | 1  | 1  | 0  |
| 14    | 0  | 1  | 1  | 1  | 0  |
| 15    | 1  | 1  | 1  | 1  | 0  |
| 16    | 0  | 0  | 0  | 0  | 1  |



4 chained half adders  
→ 4 bit counter tied to clock cycles

 2. Sketch designs for 6:64 decoder with and without the predecoding. Comment on the pros and cons of predecoding.




Predecoding uses 16 3-input NAND gates vs non-predecoding 128  
→ both designs have same path effort  
→ predecoding is more efficient

The figure below shows a logical unit that is a part of ALU used in a microprocessor. The logical unit is designed with 2-1 multiplexers. Determine which combination of encoding inputs P0-P3 sets the logical unit to perform the following operations XNOR(A,B), XOR(A,B) and NOT(A).

| Operation | P0 | P1 | P2 | P3 |
|-----------|----|----|----|----|
| XOR(A,B)  | 0  | 1  | 1  | 0  |
| XNOR(A,B) | 1  | 0  | 0  | 1  |
| NOT(A)    | 1  | 1  | 0  | 0  |

| Operation | P0 | P1 | P2 | P3 |
|-----------|----|----|----|----|
| XOR(A,B)  | 0  | 1  | 1  | 0  |
| XNOR(A,B) | 1  | 0  | 0  | 1  |
| NOT(A)    | 1  | 1  | 0  | 0  |

 

| A | B | Y              |
|---|---|----------------|
| 0 | 0 | P <sub>0</sub> |
| 0 | 1 | P <sub>1</sub> |
| 1 | 0 | P <sub>2</sub> |
| 1 | 1 | P <sub>3</sub> |

| XOR(A,B) | Y              | XNOR(A,B) |
|----------|----------------|-----------|
| 0        | P <sub>0</sub> | 1         |
| 1        | P <sub>1</sub> | 0         |
| 1        | P <sub>2</sub> | 0         |
| 0        | P <sub>3</sub> | 1         |

| Y              | NOT(A) |
|----------------|--------|
| P <sub>0</sub> | 1      |
| P <sub>1</sub> | 1      |
| P <sub>2</sub> | 0      |
| P <sub>3</sub> | 0      |